```
Date: January 14, 2023
                                                  carCount.sv
        /* Name: Eugene Ngo
    2
           Date: 1/13/2023
    3
           Class: EE 371
    4
           Lab 1: Parking Lot Occupancy Counter*/
        // carCount takes two inputs (inc, dec). It adds 5\mbox{'b00001} to out when inc is true, and subtracts 5\mbox{'b00001}
    6
    7
        // from out when dec is true. Out has a minimum value of 5'b00000 and a maximum value
        determined by the
        // parameter (25 by default).
    8
        module carCount #(parameter MAX=25) (inc, dec, out, full, clear, clk, reset);
    9
   10
   11
           input logic inc, dec, clk, reset;
           output logic [4:0] out; output logic full, clear;
   12
   13
   14
           // Sequential logic for counting up and counting down depending on the input.
   15
   16
           always_ff @(posedge clk) begin
              if (reset) begin
  out <= 5'b00000;
  full <= 1'b0;</pre>
   17
   18
   19
   20
                  clear <= 1'b0;
   21
               end
  22
23
              else if (inc & out < MAX) begin //increment when not at max</pre>
                  out <= out + 5'b00001;
   24
25
                  clear <= 1'b0;
  26
27
               else if (dec & out > 5'b00000) begin // decrement when not at min
                  out <= out - 5'b00001;
   28
29
                  full <= 1'b0;
               end
   30
               else if (out == MAX) begin // hold value at max, output full
   31
32
33
                  out_<= MAX;
                  full <= 1'b1;
   34
               else if (out == 5'b00000) begin // hold value at min, output clear
   35
                  out <= 5'b00000;
   36
                  clear <= 1'b1;
   37
              end
   38
              else
   39
                  out <= out; // hold value otherwise
   40
           end // always_ff
   41
   42
        endmodule
   43
   44
        // carCount_testbench tests all expected, unexpected, and edgecase behaviors
   45
        module carCount_testbench();
           logic inc, dec, full, clear, reset;
logic [4:0] out;
   46
   47
   48
           logic CLOCK_50;
   49
   50
           carCount #(5) dut (.inc, .dec, .out, .full, .clear, .clk(CLOCK_50), .reset);
   51
   52
           // Setting up the clock.
   53
           parameter CLOCK_PERIOD = 100;
   54
55
           initial begin
               CLOCK_50 \ll 0;
   56
               forever #(CLOCK_PERIOD/2) CLOCK_50 <= ~CLOCK_50; // toggle the clock forever</pre>
   57
           end // initial
   58
   59
           initial begin
                                                  repeat(3) @(posedge CLOCK_50); // reset
   60
               reset \leftarrow 1;
                            61
               reset \leftarrow 0; inc \leftarrow 1;
   62
   63
               $stop;
   64
           end
   65
        endmodule // counter_testbench
```