

```

1  /* Name: Eugene Ngo
2  Date: 1/13/2023
3  Class: EE 371
4  Lab 6
5  Taken from Lab 1 and adapted for lab 6 task 1 */
6
7  // seg7 outputs correct decimal value to hex displays based on the output given by the
  counter.
8  // It also displays "FULL" and "CLEAR" according to the indicator outputs given by the
  counter.
9  module seg7 (in, full, clear, hexout0, hexout1, hexout2, hexout3, hexout4, hexout5);
10
11     input logic full, clear;
12     input logic [4:0] in;
13     output logic [6:0] hexout0, hexout1, hexout2, hexout3, hexout4, hexout5;
14
15     // Assigning hex display variables on necessary numbers.
16     logic [6:0] hex0, hex1, hex2, hex3, hex4, hex5, hex6, hex7, hex8, hex9;
17     assign hex0 = 7'b1000000; // 0
18     assign hex1 = 7'b1111001; // 1
19     assign hex2 = 7'b0100100; // 2
20     assign hex3 = 7'b0110000; // 3
21     assign hex4 = 7'b0011001; // 4
22     assign hex5 = 7'b0010010; // 5
23     assign hex6 = 7'b0000010; // 6
24     assign hex7 = 7'b1111000; // 7
25     assign hex8 = 7'b0000000; // 8
26     assign hex9 = 7'b0010000; // 9
27
28     // Assigning hex display variables on necessary letters.
29     logic [6:0] hexf, hexu, hexl, hexc, hexe, hexa, hexr, hexoff;
30     assign hexf = 7'b0001110; // F
31     assign hexu = 7'b1000001; // U
32     assign hexl = 7'b1000111; // L
33     assign hexc = 7'b1000110; // C
34     assign hexe = 7'b0000110; // E
35     assign hexa = 7'b0001000; // A
36     assign hexr = 7'b0101111; // R
37     assign hexoff = 7'b1111111; // off
38
39     // Logic for hexout0: 26 different cases for 26 numbers. (0-25)
40     always_comb begin
41         case(in)
42             5'b00000: hexout0 = hex0;
43             5'b00001: hexout0 = hex1;
44             5'b00010: hexout0 = hex2;
45             5'b00011: hexout0 = hex3;
46             5'b00100: hexout0 = hex4;
47             5'b00101: hexout0 = hex5;
48             5'b00110: hexout0 = hex6;
49             5'b00111: hexout0 = hex7;
50             5'b01000: hexout0 = hex8;
51             5'b01001: hexout0 = hex9;
52             5'b01010: hexout0 = hex0;
53             5'b01011: hexout0 = hex1;
54             5'b01100: hexout0 = hex2;
55             5'b01101: hexout0 = hex3;
56             5'b01110: hexout0 = hex4;
57             5'b01111: hexout0 = hex5;
58             5'b10000: hexout0 = hex6;
59             5'b10001: hexout0 = hex7;
60             5'b10010: hexout0 = hex8;
61             5'b10011: hexout0 = hex9;
62             5'b10100: hexout0 = hex0;
63             5'b10101: hexout0 = hex1;
64             5'b10110: hexout0 = hex2;
65             5'b10111: hexout0 = hex3;
66             5'b11000: hexout0 = hex4;
67             5'b11001: hexout0 = hex5;
68             default: hexout0 = 7'bx;
69         endcase
70     end // always_comb
71

```

```

72 // Logic for hexout1: 26 different cases for 26 numbers. (0-25)
73 always_comb begin
74     case(in)
75         5'b00000: hexout1 = hexr;
76         5'b00001: hexout1 = hexoff;
77         5'b00010: hexout1 = hexoff;
78         5'b00011: hexout1 = hexoff;
79         5'b00100: hexout1 = hexoff;
80         5'b00101: hexout1 = hexoff;
81         5'b00110: hexout1 = hexoff;
82         5'b00111: hexout1 = hexoff;
83         5'b01000: hexout1 = hexoff;
84         5'b01001: hexout1 = hexoff;
85         5'b01010: hexout1 = hex1;
86         5'b01011: hexout1 = hex1;
87         5'b01100: hexout1 = hex1;
88         5'b01101: hexout1 = hex1;
89         5'b01110: hexout1 = hex1;
90         5'b01111: hexout1 = hex1;
91         5'b10000: hexout1 = hex1;
92         5'b10001: hexout1 = hex1;
93         5'b10010: hexout1 = hex1;
94         5'b10011: hexout1 = hex1;
95         5'b10100: hexout1 = hex2;
96         5'b10101: hexout1 = hex2;
97         5'b10110: hexout1 = hex2;
98         5'b10111: hexout1 = hex2;
99         5'b11000: hexout1 = hex2;
100        5'b11001: hexout1 = hex2;
101        default: hexout1 = 7'bx;
102    endcase
103 end // always_comb
104
105 // Logic for hexout5 - hexout2: display letters when full or clear, turn off otherwise.
106 always_comb begin
107     if (full) begin
108         hexout5 = hexf;
109         hexout4 = hexu;
110         hexout3 = hexl;
111         hexout2 = hexl;
112     end
113     else if (clear) begin
114         hexout5 = hexc;
115         hexout4 = hexl;
116         hexout3 = hexe;
117         hexout2 = hexa;
118     end
119     else begin
120         hexout5 = hexoff;
121         hexout4 = hexoff;
122         hexout3 = hexoff;
123         hexout2 = hexoff;
124     end
125 end // always_comb
126
127 endmodule // seg7
128
129 // seg7_testbench tests all expected, unexpected, and edgecase behaviors
130 module seg7_testbench();
131     logic full, clear;
132     logic [4:0] in;
133     logic [6:0] hexout0, hexout1, hexout2, hexout3, hexout4, hexout5;
134
135     seg7 dut (.in, .full, .clear, .hexout0, .hexout1, .hexout2, .hexout3, .hexout4, .hexout5);
136
137     initial begin
138         in = '0; clear = 1; full = 0; #10; // testing clear output
139         in = 5'b11001; clear = 0; full = 1; #10; // testing full output
140         in = 5'b10011; clear = 0; full = 0; #10; // testing regular output
141         $stop;
142     end // initial
143 endmodule // seg7_testbench

```