

```

1  /* Name: Eugene Ngo
2  Date: 1/13/2023
3  Class: EE 371
4  Lab 1: Parking Lot Occupancy Counter*/
5
6  // seg7 outputs correct decimal value to hex displays based on the output given by the
   counter.
7  // It also displays "FULL" and "CLEAR" according to the indicator outputs given by the
   counter.
8  module seg7 (in, full, clear, hexout0, hexout1, hexout2, hexout3, hexout4, hexout5);
9
10     input logic full, clear;
11     input logic [4:0] in;
12     output logic [6:0] hexout0, hexout1, hexout2, hexout3, hexout4, hexout5;
13
14     // Assigning hex display variables on necessary numbers.
15     logic [6:0] hex0, hex1, hex2, hex3, hex4, hex5, hex6, hex7, hex8, hex9;
16     assign hex0 = 7'b1000000; // 0
17     assign hex1 = 7'b1111001; // 1
18     assign hex2 = 7'b0100100; // 2
19     assign hex3 = 7'b0110000; // 3
20     assign hex4 = 7'b0011001; // 4
21     assign hex5 = 7'b0010010; // 5
22     assign hex6 = 7'b0000010; // 6
23     assign hex7 = 7'b1111000; // 7
24     assign hex8 = 7'b0000000; // 8
25     assign hex9 = 7'b0010000; // 9
26
27     // Assigning hex display variables on necessary letters.
28     logic [6:0] hexf, hexu, hexl, hexc, hexe, hexa, hexr, hexoff;
29     assign hexf = 7'b0001110; // F
30     assign hexu = 7'b1000001; // U
31     assign hexl = 7'b1000111; // L
32     assign hexc = 7'b1000110; // C
33     assign hexe = 7'b0000110; // E
34     assign hexa = 7'b0001000; // A
35     assign hexr = 7'b0101111; // R
36     assign hexoff = 7'b1111111; // off
37
38     // Logic for hexout0: 26 different cases for 26 numbers. (0-25)
39     always_comb begin
40         case(in)
41             5'b00000: hexout0 = hex0;
42             5'b00001: hexout0 = hex1;
43             5'b00010: hexout0 = hex2;
44             5'b00011: hexout0 = hex3;
45             5'b00100: hexout0 = hex4;
46             5'b00101: hexout0 = hex5;
47             5'b00110: hexout0 = hex6;
48             5'b00111: hexout0 = hex7;
49             5'b01000: hexout0 = hex8;
50             5'b01001: hexout0 = hex9;
51             5'b01010: hexout0 = hex0;
52             5'b01011: hexout0 = hex1;
53             5'b01100: hexout0 = hex2;
54             5'b01101: hexout0 = hex3;
55             5'b01110: hexout0 = hex4;
56             5'b01111: hexout0 = hex5;
57             5'b10000: hexout0 = hex6;
58             5'b10001: hexout0 = hex7;
59             5'b10010: hexout0 = hex8;
60             5'b10011: hexout0 = hex9;
61             5'b10100: hexout0 = hex0;
62             5'b10101: hexout0 = hex1;
63             5'b10110: hexout0 = hex2;
64             5'b10111: hexout0 = hex3;
65             5'b11000: hexout0 = hex4;
66             5'b11001: hexout0 = hex5;
67             default: hexout0 = 7'bx;
68         endcase
69     end // always_comb
70
71     // Logic for hexout1: 26 different cases for 26 numbers. (0-25)

```

```

72     always_comb begin
73         case(in)
74             5'b00000: hexout1 = hexr;
75             5'b00001: hexout1 = hexoff;
76             5'b00010: hexout1 = hexoff;
77             5'b00011: hexout1 = hexoff;
78             5'b00100: hexout1 = hexoff;
79             5'b00101: hexout1 = hexoff;
80             5'b00110: hexout1 = hexoff;
81             5'b00111: hexout1 = hexoff;
82             5'b01000: hexout1 = hexoff;
83             5'b01001: hexout1 = hexoff;
84             5'b01010: hexout1 = hex1;
85             5'b01011: hexout1 = hex1;
86             5'b01100: hexout1 = hex1;
87             5'b01101: hexout1 = hex1;
88             5'b01110: hexout1 = hex1;
89             5'b01111: hexout1 = hex1;
90             5'b10000: hexout1 = hex1;
91             5'b10001: hexout1 = hex1;
92             5'b10010: hexout1 = hex1;
93             5'b10011: hexout1 = hex1;
94             5'b10100: hexout1 = hex2;
95             5'b10101: hexout1 = hex2;
96             5'b10110: hexout1 = hex2;
97             5'b10111: hexout1 = hex2;
98             5'b11000: hexout1 = hex2;
99             5'b11001: hexout1 = hex2;
100            default: hexout1 = 7'bx;
101        endcase
102    end // always_comb
103
104    // Logic for hexout5 - hexout2: display letters when full or clear, turn off otherwise.
105    always_comb begin
106        if (full) begin
107            hexout5 = hexf;
108            hexout4 = hexu;
109            hexout3 = hexl;
110            hexout2 = hexl;
111        end
112        else if (clear) begin
113            hexout5 = hexc;
114            hexout4 = hexl;
115            hexout3 = hexe;
116            hexout2 = hexa;
117        end
118        else begin
119            hexout5 = hexoff;
120            hexout4 = hexoff;
121            hexout3 = hexoff;
122            hexout2 = hexoff;
123        end
124    end // always_comb
125
126 endmodule // seg7
127
128 // seg7_testbench tests all expected, unexpected, and edgecase behaviors
129 module seg7_testbench();
130     logic full, clear;
131     logic [4:0] in;
132     logic [6:0] hexout0, hexout1, hexout2, hexout3, hexout4, hexout5;
133
134     seg7 dut (.in, .full, .clear, .hexout0, .hexout1, .hexout2, .hexout3, .hexout4, .hexout5);
135
136     initial begin
137         in = '0; clear = 1; full = 0; #10; // testing clear output
138         in = 5'b11001; clear = 0; full = 1; #10; // testing full output
139         in = 5'b10011; clear = 0; full = 0; #10; // testing regular output
140         $stop;
141     end // initial
142 endmodule // seg7_testbench

```